

II B. Tech I Semester Supplementary Examinations, May/June - 2016
ELECTRICAL CIRCUIT ANALYSIS - II
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **THREE** Questions from **Part-B**
- ~~~~~

PART - A

1. a) Write the equations for different types of powers in three phase circuits and write the equation for power factor in three phase systems. (3M)
- b) Explain how can a watt meter is used to measure reactive power. (3M)
- c) Give the application of h-parameter and also state the relation between h-parameter with transmission parameter. (4M)
- d) Write four properties of Laplace transform. (4M)
- e) What do we mean by Network synthesis? How is it different from network analysis. (4M)
- f) Write four properties of fourier transform (4M)

PART - B

2. a) Three impedances each of $(5-j6) \Omega$ are connected in delta across a 3ph, 250V, 50 Hz balanced supply. Calculate the line and phase currents in the delta connected load. (8M)
- b) Explain how three phase active and reactive power is measured in three phase systems. (8M)
3. a) An unbalanced four wire, star connected load has a balanced voltage of 400V, the loads are $Z_1 = (4+j8)$ ohms; $Z_2 = (3+j4)$ ohms; $Z_3 = (15+j20)$ ohms. Calculate the neutral current and the total power. (8M)
- b) Explain how three phase power is measured using two watt meter method. (8M)
4. a) For an RL series circuit, a sinusoidal voltage of $v(t) = V_m \sin(\omega t + \phi)$ is applied at $t=0$. Find the expression for transient current. (8M)
- b) Explain the advantages of Laplace transformation and Obtain Laplace transform off $(t) = \exp(at)$ (8M)



5. a) What are Y-Parameters and Z-Parameters. Derive the Expression for Z Parameters in terms of Y-parameters and vice – versa. (8M)
- b) Determine the Y- parameters of the network shown in Figure 1. (8M)

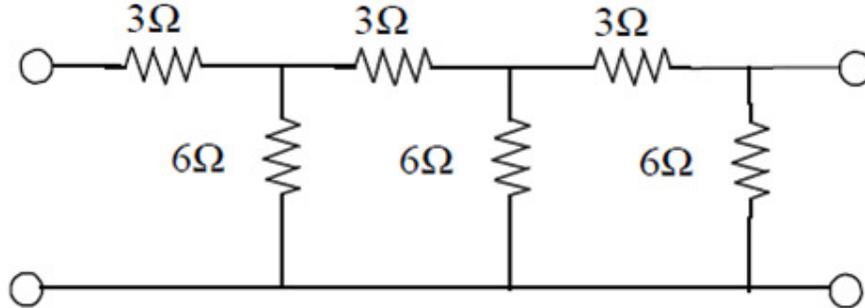


Figure 1

6. a) Determine the Foster's first form after synthesizing the RL driving point impedance function. $Z(S) = [(s+1)(s+3)] / [(S+2)(S+4)]$ (8M)
- b) Synthesize the LC driving point impedance function (8M)

$$Z(s) = \frac{10s+12}{4s^2+s+8}$$

7. a) Determine the Fourier series of the repetitive waveform shown in Figure 2 up to the 7th harmonic when the repetition time $T=25\pi$ ms. (8M)

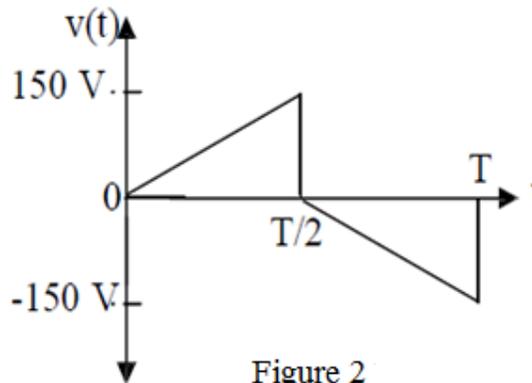


Figure 2

- b) Obtain the exponential Fourier series for the periodic function in Figure 3, and plot the amplitude and phase spectra. (8M)

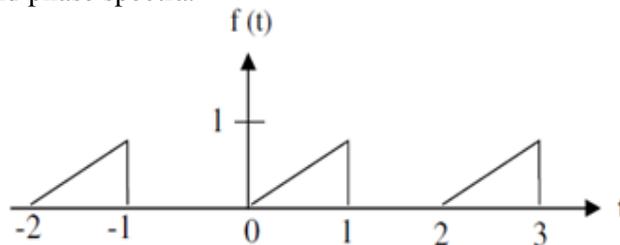


Figure 3

